
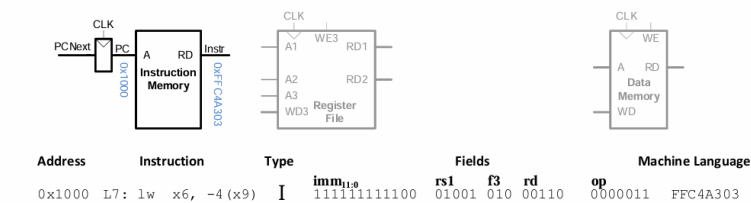



STEP 1: Fetch instruction

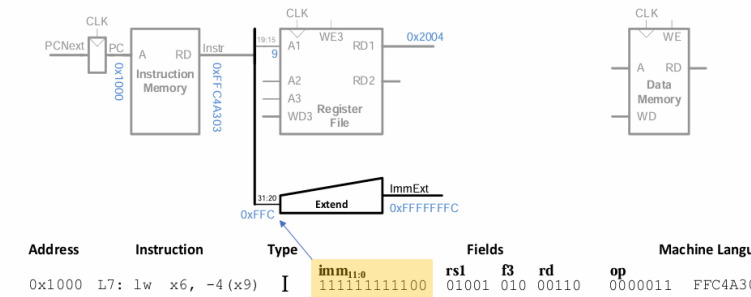


STEP 3: Extend the immediate



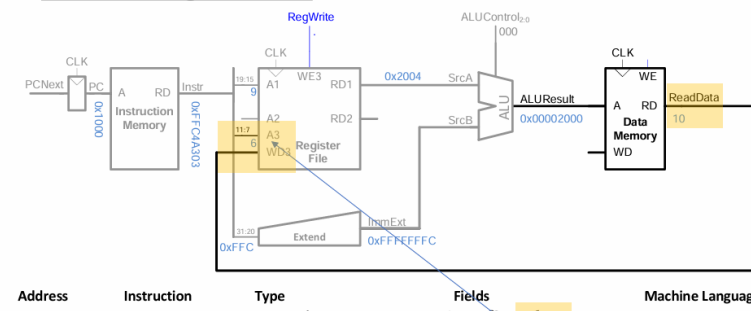
STEP 5: Read data from memory and write it back to register file



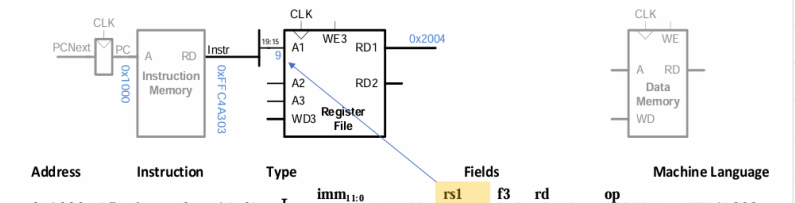
STEP 2: Read source operand (rs1) from Register File (RF)




STEP 4: Compute the memory address

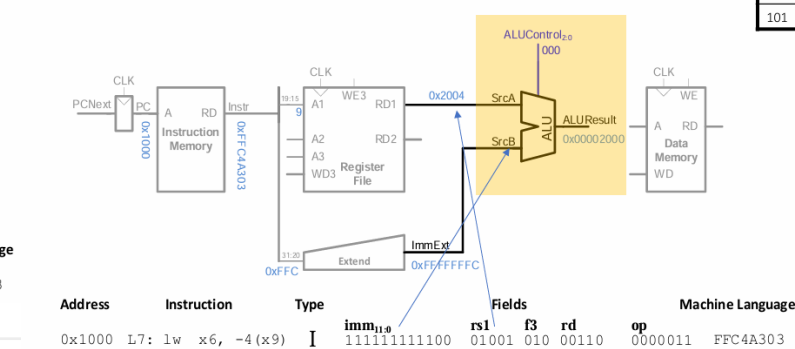

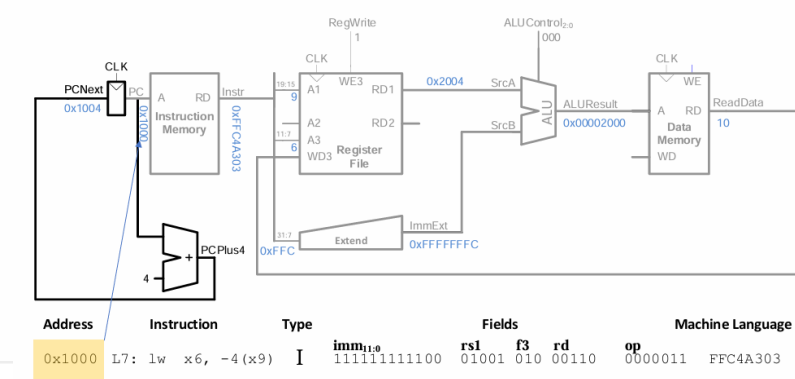
STEP 6: Determine address of next instruction




Single-Cycle Datapath: sw

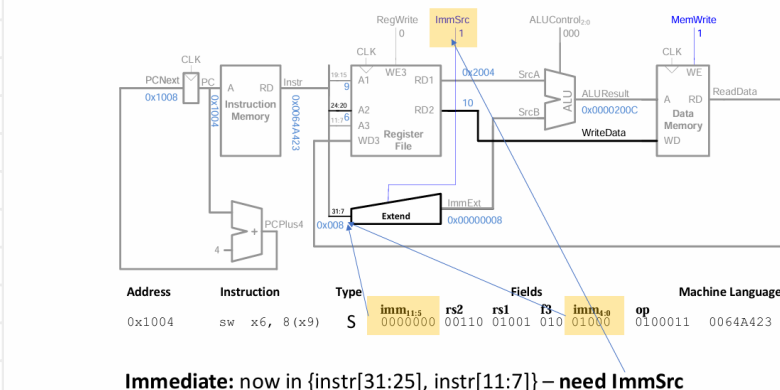

Single-Cycle Datapath: beq

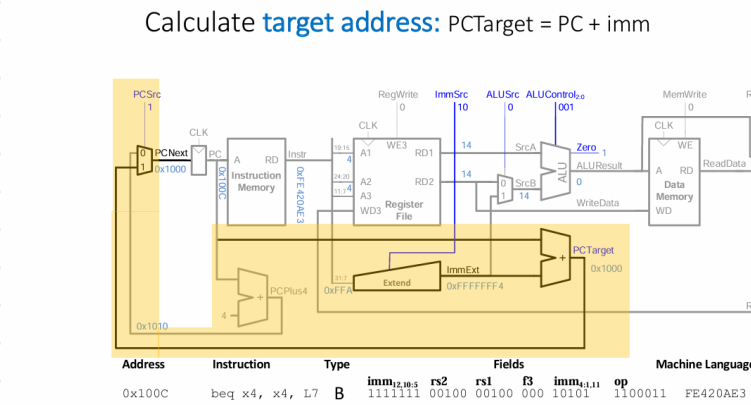

NEXT INSTRUCTION: or operation

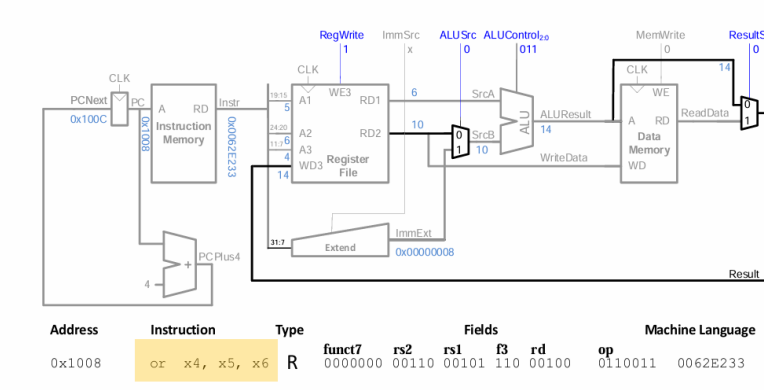

ALUControl _{2:0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

Extended Functionality: addi

op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
19	I-type	1	00	1	0	0	0	10

